

# **Logic Design & Computer Organization Lab**

## **Assignment 1 - IC Testing**

Name : Gopal Saraf

Class : SE 09


Batch : H9

Roll No : 23168

# 74HC00

## NAND GATE

### Pin Assignments

 

### Truth Table


Input		Output
A	B	$Y = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

# 74HC02

## NOR GATE

---

### Pin Assignments

 

### Truth Table

Input		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0


---

# 74HC08

## AND GATE

---

### Pin Assignments

 

### Truth Table

Input		Output
A	B	$Y=A.B$
0	0	0
0	1	0
1	0	0
1	1	1


---

# 74HC32

## OR GATE

---

### Pin Assignments

 

### Truth Table

Input		Output
A	B	$Y=A+B$
0	0	0
0	1	1
1	0	1
1	1	1


---

# 74HC86

## XOR GATE

---

### Pin Assignments

 

### Truth Table

INPUTS		OUTPUT
a	b	A XOR B
0	0	0
1	0	1
0	1	1
1	1	0

---

# Tinkercad Circuit :

